

Strong Arm Sense Amplifier

Group Number: 22



INDRAPRASTHA INSTITUTE *of*
INFORMATION TECHNOLOGY
DELHI

Group Members :



- Deepank – 21107
- Tarun – 21106
- Anushka – MT21187
- Sudhanshu – MT21212

Schematic + Sizing





NMOS : 0.54u/0.06u [Footer+Input+Latch]


PMOS : 0.135u/0.06u [Precharge+Latch]

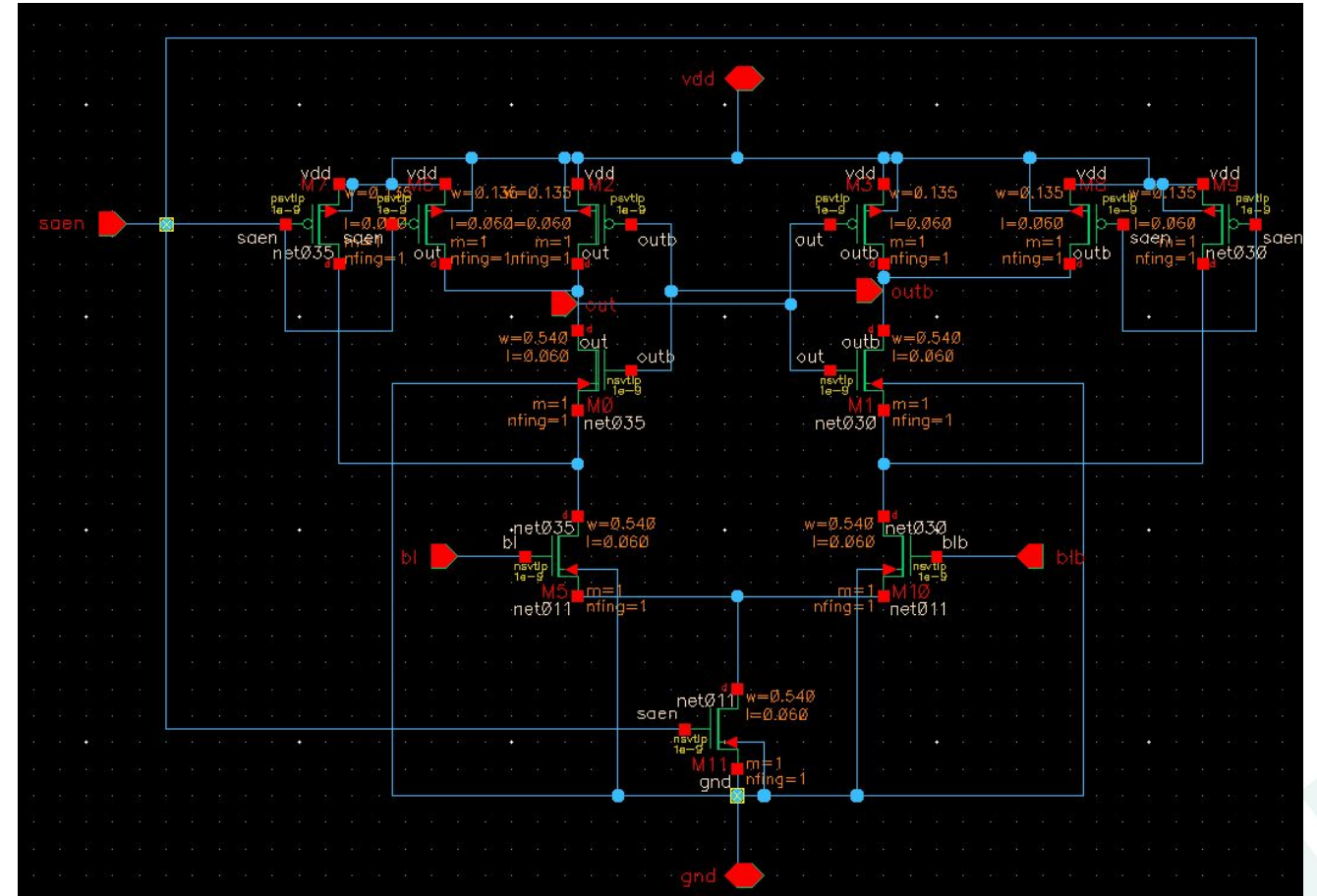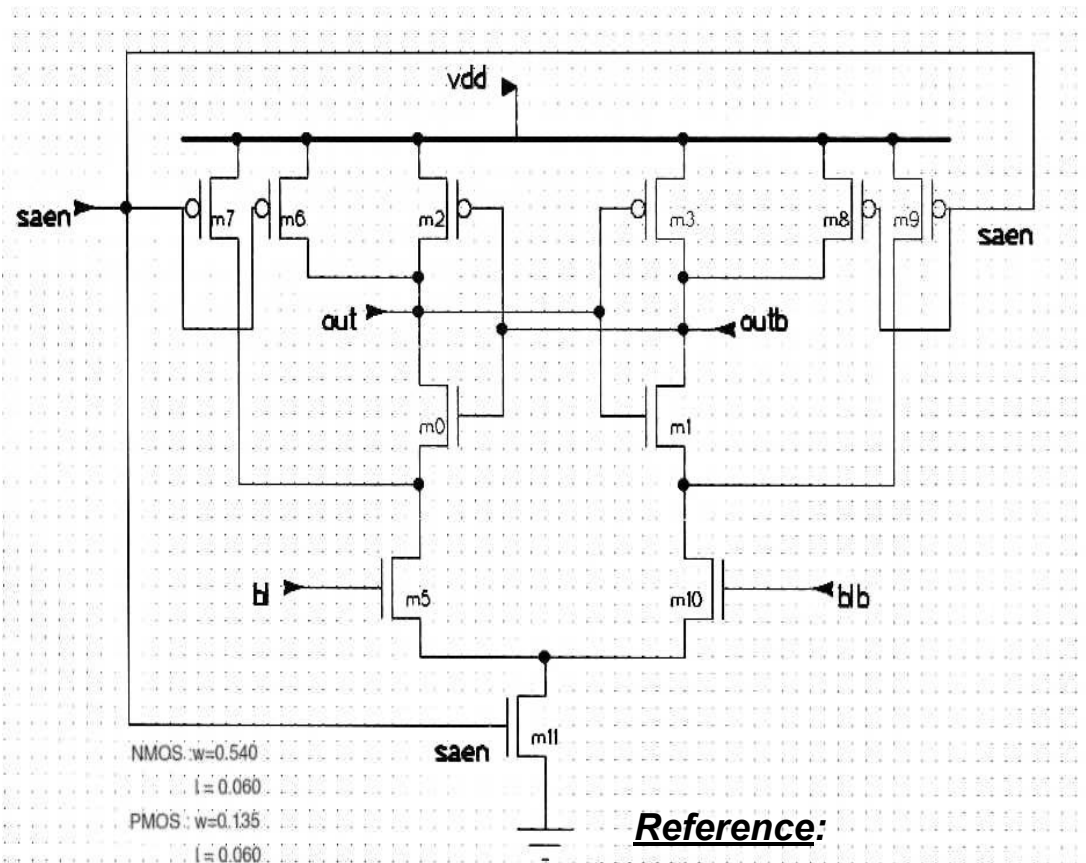

Layout | Area = $3.8\mu \times 3.53\mu = 13.414\mu m^2$

  


Simulation Waveform | Pre v/s Post

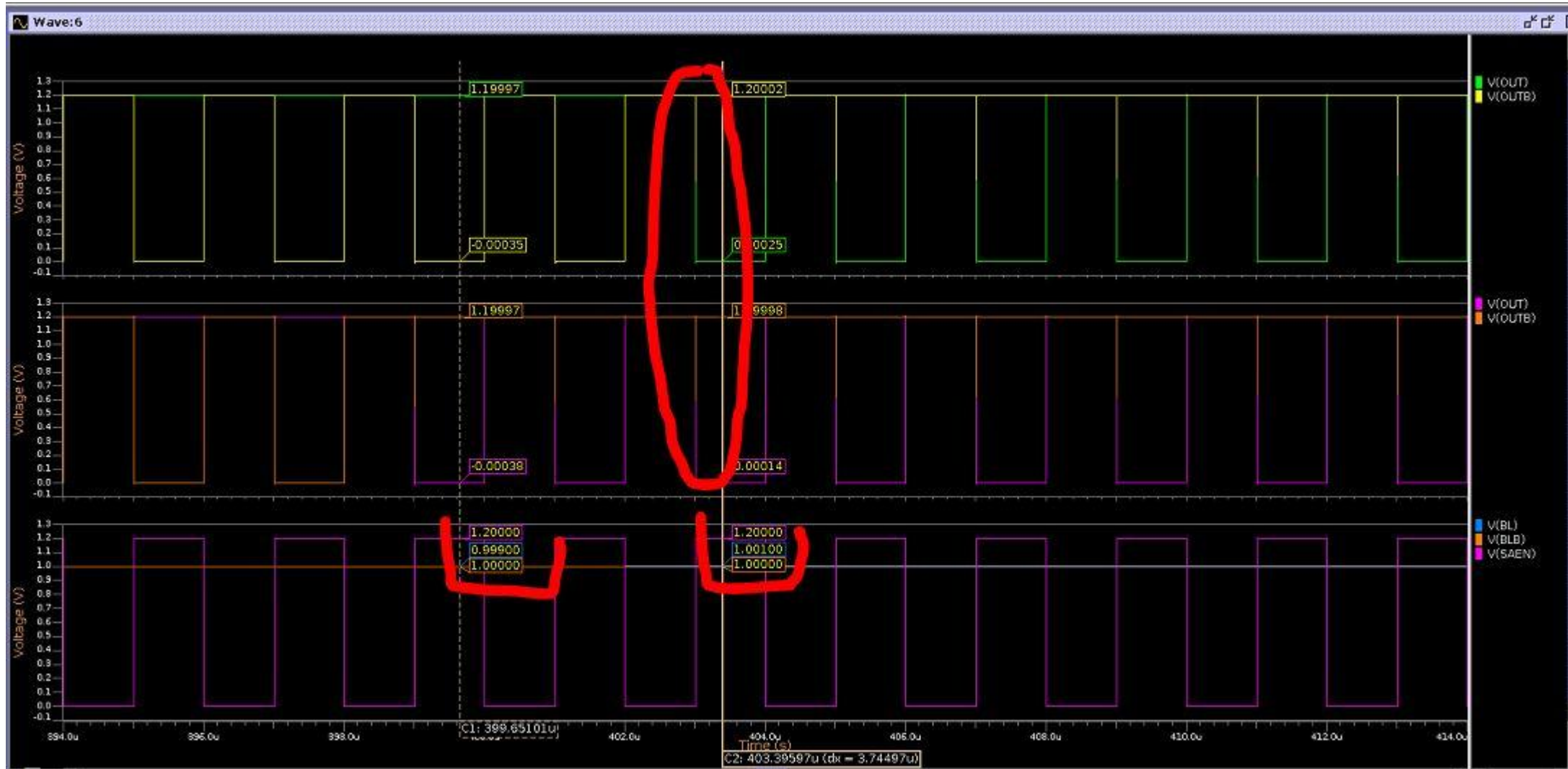


PVT : TT/1.2V/25C

Simulation Waveform | Pre v/s Post

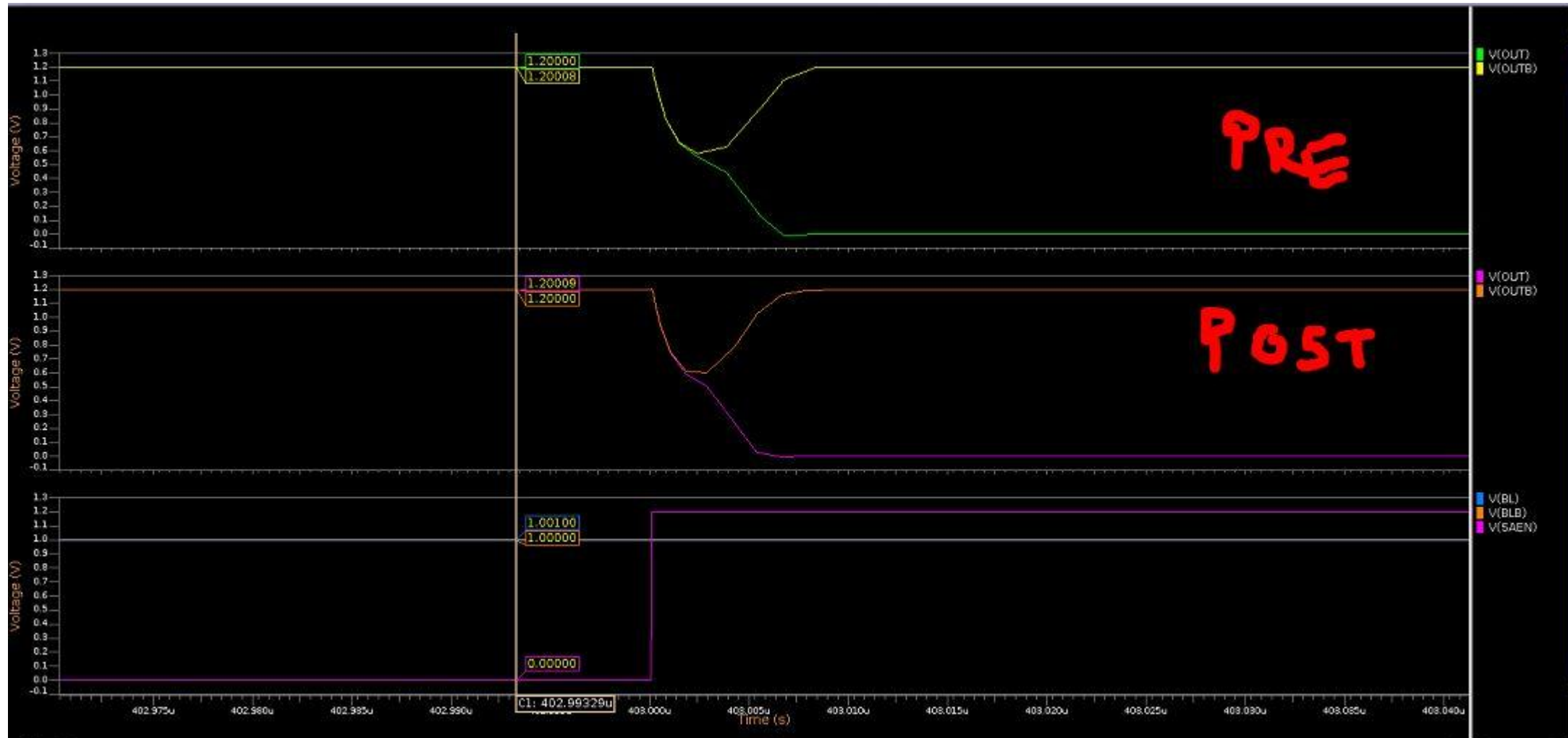

PVT : TT/1.2V/25C

Simulation Waveform | Pre v/s Post

 


PVT : TT/1.2V/25C

Offset Analysis




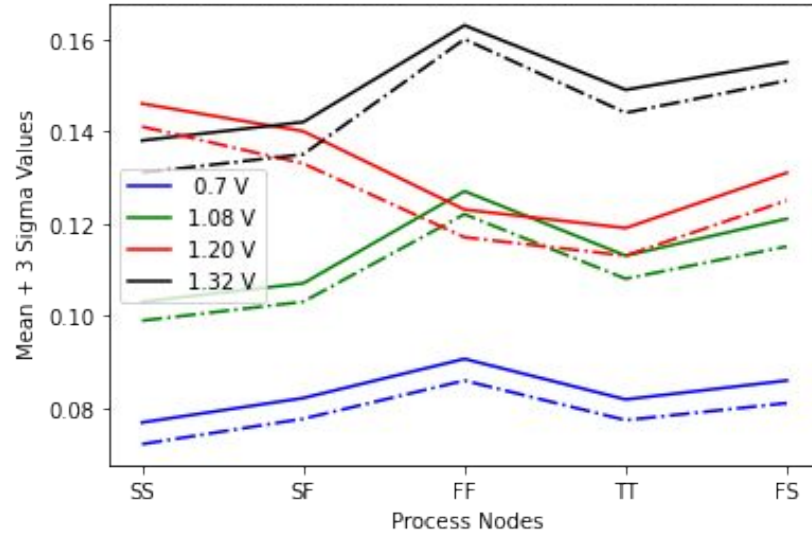Offset Variation by supply voltage at 25 C (--- = Post Layout Results)




—	PreLayout
— · —	PostLayout

Offset Variation by Temperature at 1.2 V

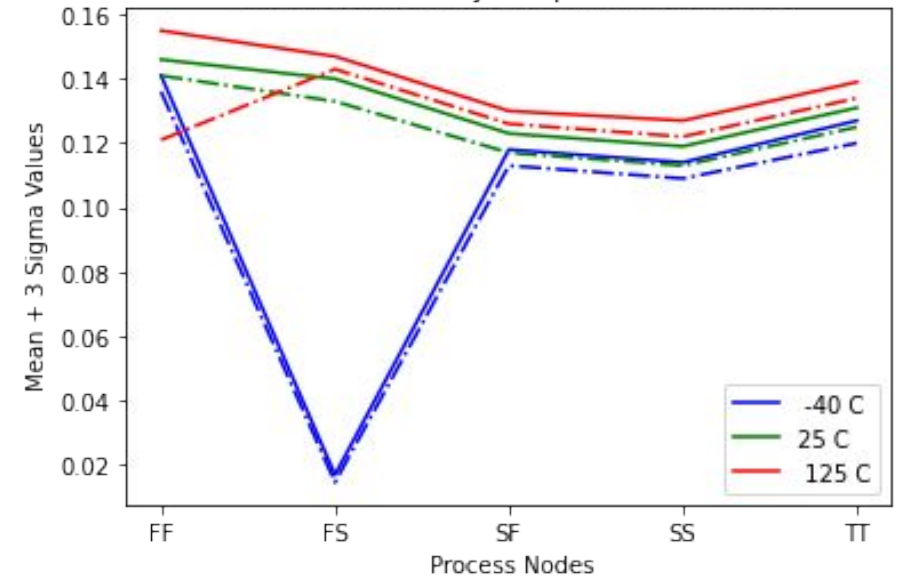

Offset Variation (TT)

 

Offset Analysis



- Worst Case PVT: FF/1.32V/125C
 - Prelayout @ Worst Case = 167mV
 - Postlayout @ Worst Case = 169mV
- Best Case PVT: FS/1.2V/-40C
 - Prelayout @ Best Case = 17mV
 - Postlayout @ Best Case = 15mV







Reaction Time Analysis



- Time V(OUT) takes to flip (i.e. drop to 10% of supply voltage) after the rising edge of SAEN(50% supply)
- Best and worst cases:

	Minimum RT	Maximum RT	RT @TT,1.2V,25C
Pre-layout	3.25ns @FF,1.32V,-40C	580ns @SS,0.7V,-40C	5.56ns
Post-layout	3.24ns @FF,1.32V,-40C	769ns @SS,0.7V,-40C	6.24ns

Reaction Time Analysis

 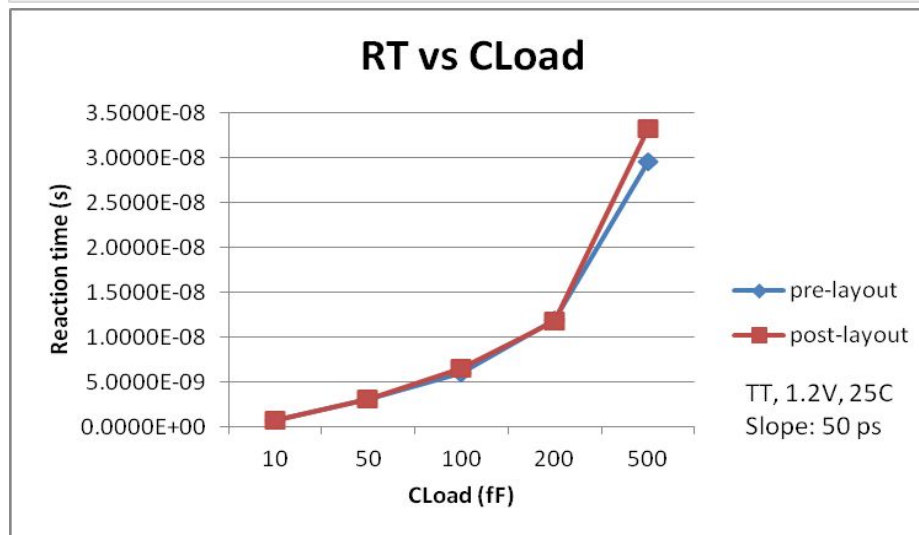  

Power Analysis



Parameter	Total Power (nW)		Leakage Power (nW)		Dynamic Power (nW)	
Worst PVT	FF/1.32V/25 C		FF/1.32V/25C		FF/1.32V/125C	
Worst PVT value	PRE 36.28	POST 36.6	PRE 34.15	POST 34.43	PRE 2.13	POST 2.2
Best PVT	SS/0.7V/-40 (FF and TT come very close)		TT/0.7V/-40 (SS close)		SS/1.32/-40	
Best PVT value	PRE 0.067	POST 0.07	PRE 0.004	POST 0.005	PRE 0.046	POST 0.05
Value at typical PVT (TT, 1.2, 25 C)	0.398	0.4	0.274	0.28	0.124	0.13

Sweep Analysis : Sizing



SS/0.7V/-40C							
Length= 0.06um							
Width_Footer (um)	Offset(m+3sd) (mV)	Width_Input (um)	Offset(m+3sd) (mV)	Width_Latch (um)	Offset(m+3sd) (mV)	Width_All (um)	Offset(m+3sd) (mV)
0.135	83	0.135	119	0.135	89	0.135	175.4
0.54	86	0.54	60	0.54	86	0.54	89.8
1.08	86	1.08	44	1.08	83	1.08	62.4

- **Area** = 13.414 μm^2
- **Performance** =
 - Offset follows expected trend only at **1.2V/25C**, i.e., very low value at **FF** and highest value at **SS**
 - Reaction Time follows expected trend also, lowest at FF/1.32V/-40C and highest at SS/0.7V/-40C
- **Power** = Maximum power occurs at FF/1.32V, **25C** for leak+avg & **125C** for dynamic
- **Characterizing design** :
 - PVT = TT/1.2V/25C with following Performance metrics:
 - Offset = 125mV(Post) & 131mV(Pre)
 - Reaction Time = 6.24ns(Post) & 5.56ns(Pre)
 - Avg. Power = 110.5nW(Post) & 99.7(pre)

- Deepank = Setup + Offset Analysis + Sizing + Layout
- Tarun = Power Analysis + Stick Diagram + Layout
- Anushka = Timing Analysis + Sizing
- Sudhanshu = XCircuit + Power Analysis

Shortcomings & Future Scope:

- Length Should have been taken larger to reduce SD
- Common Centroid should be used to minimise systematic offset
- Output nodes must be connected to inverter instead of a capacitance
- Length of input NMOS should be larger than other NMOS to increase current and reduce effect of mismatches hence decreasing the offset.
- Investigating reason for unexpected trend and fixing it.
- Comparison with design without Stack PMOS instead NMOS used to balance internal node in precharge.

